
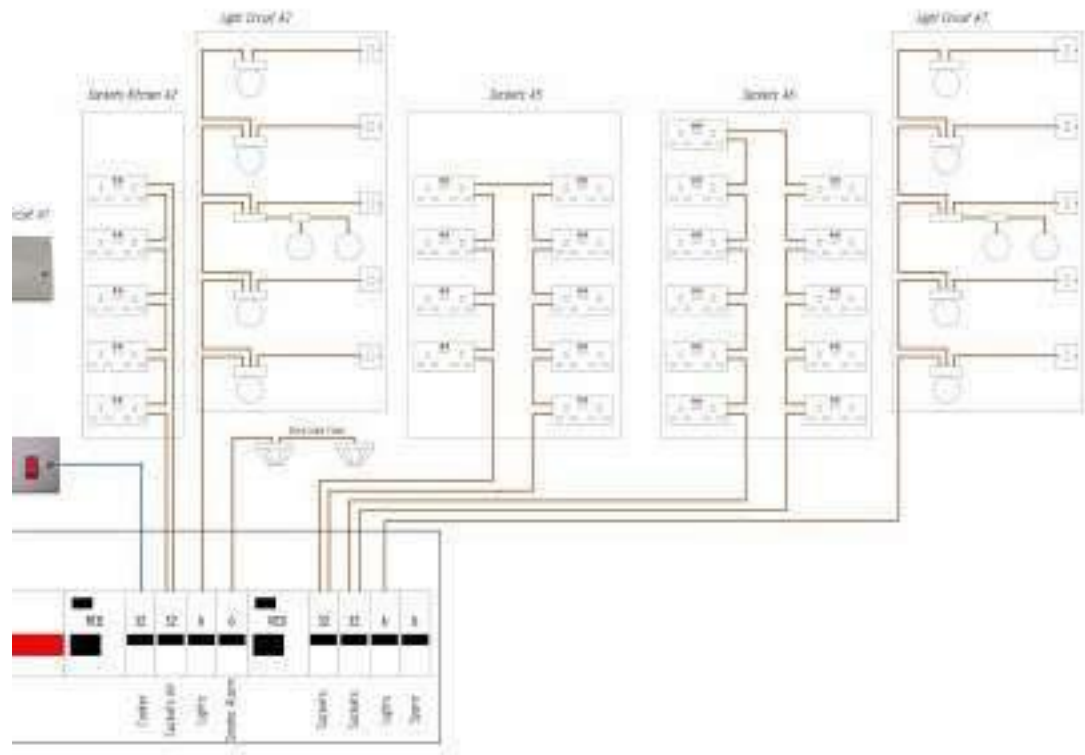



Wiring Circuit Diagram

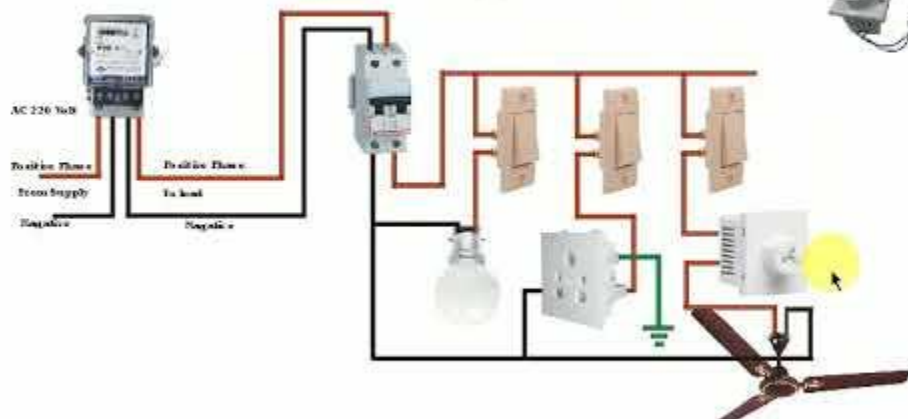

A.K AK Engineers
Presents

Electrical wiring tutorial Part 3



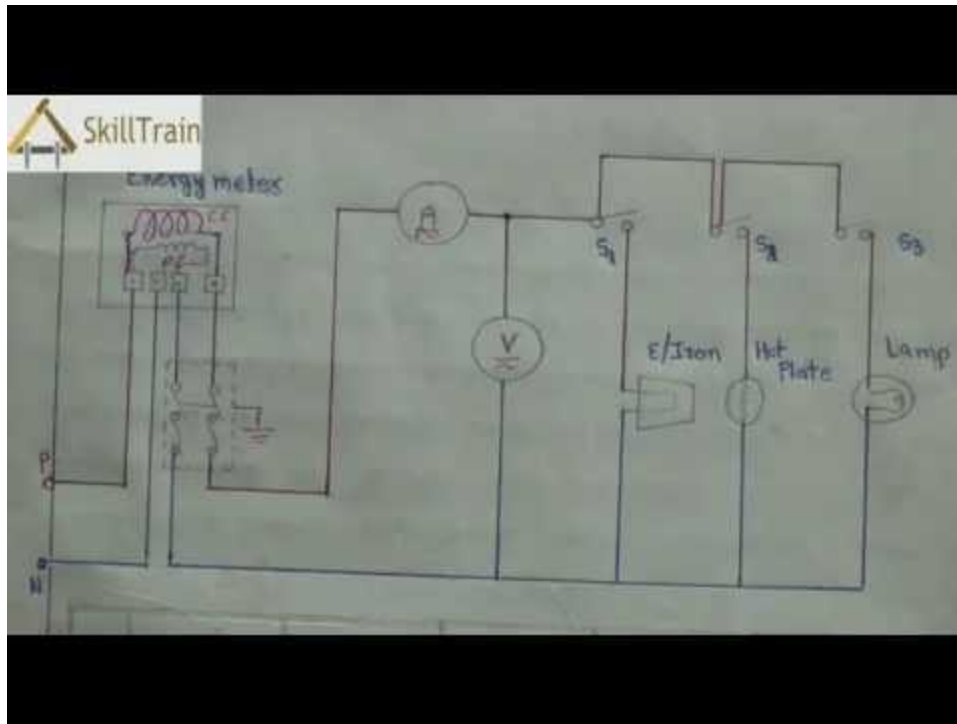


घर की वायरिंग

www.electguru.com



करवाते समय
ध्यान रखने
वाली बातें


The Inlet "Outlet"

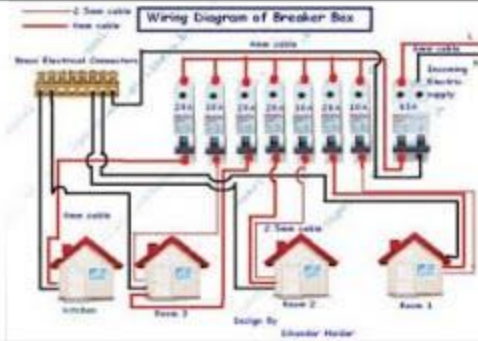

Three phase house wiring in हिन्दी

— 2.5mm cable
— 4mm cable

Wiring Diagram of Breaker Box

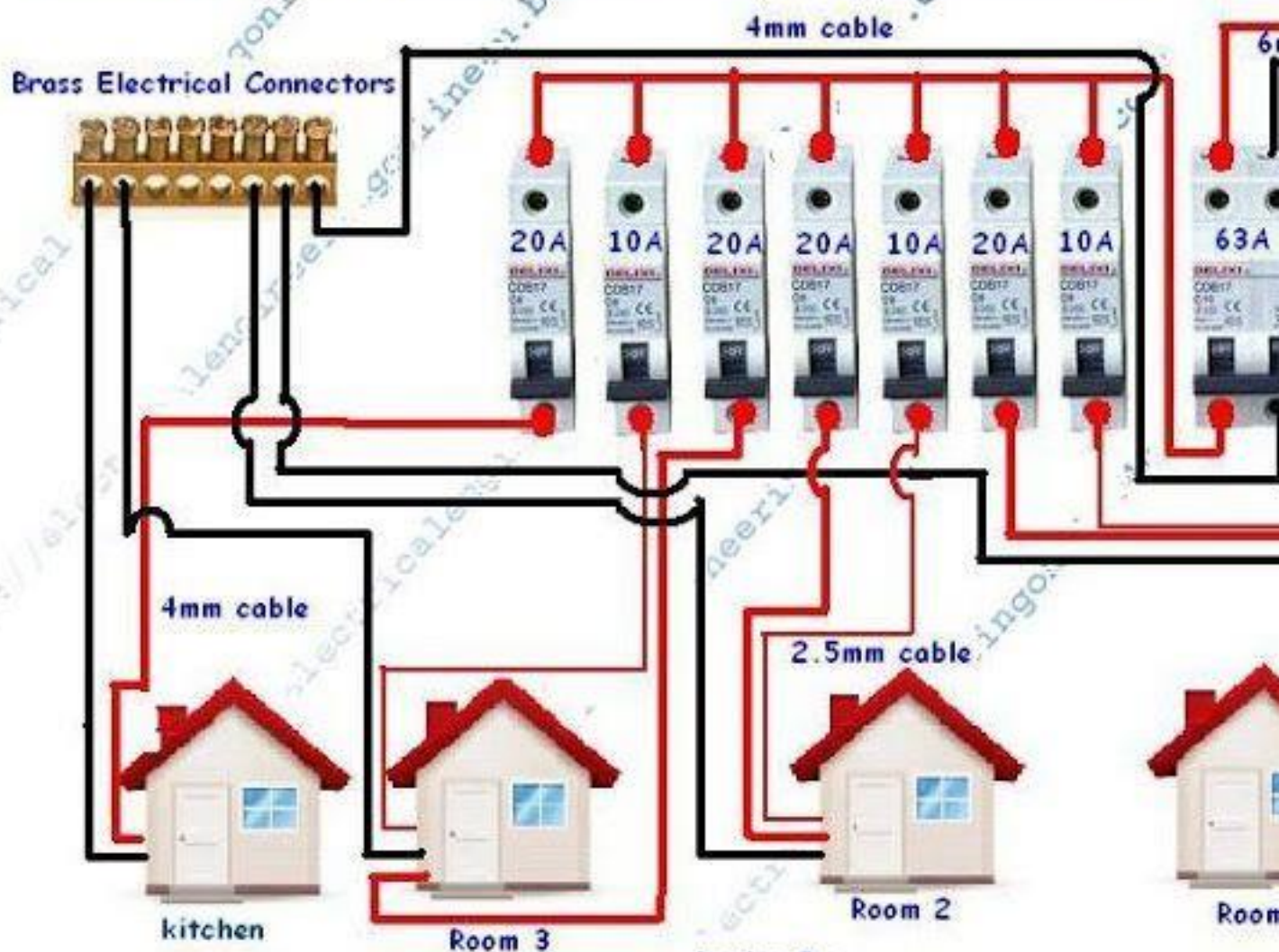

Design By
Sikandar Haidar